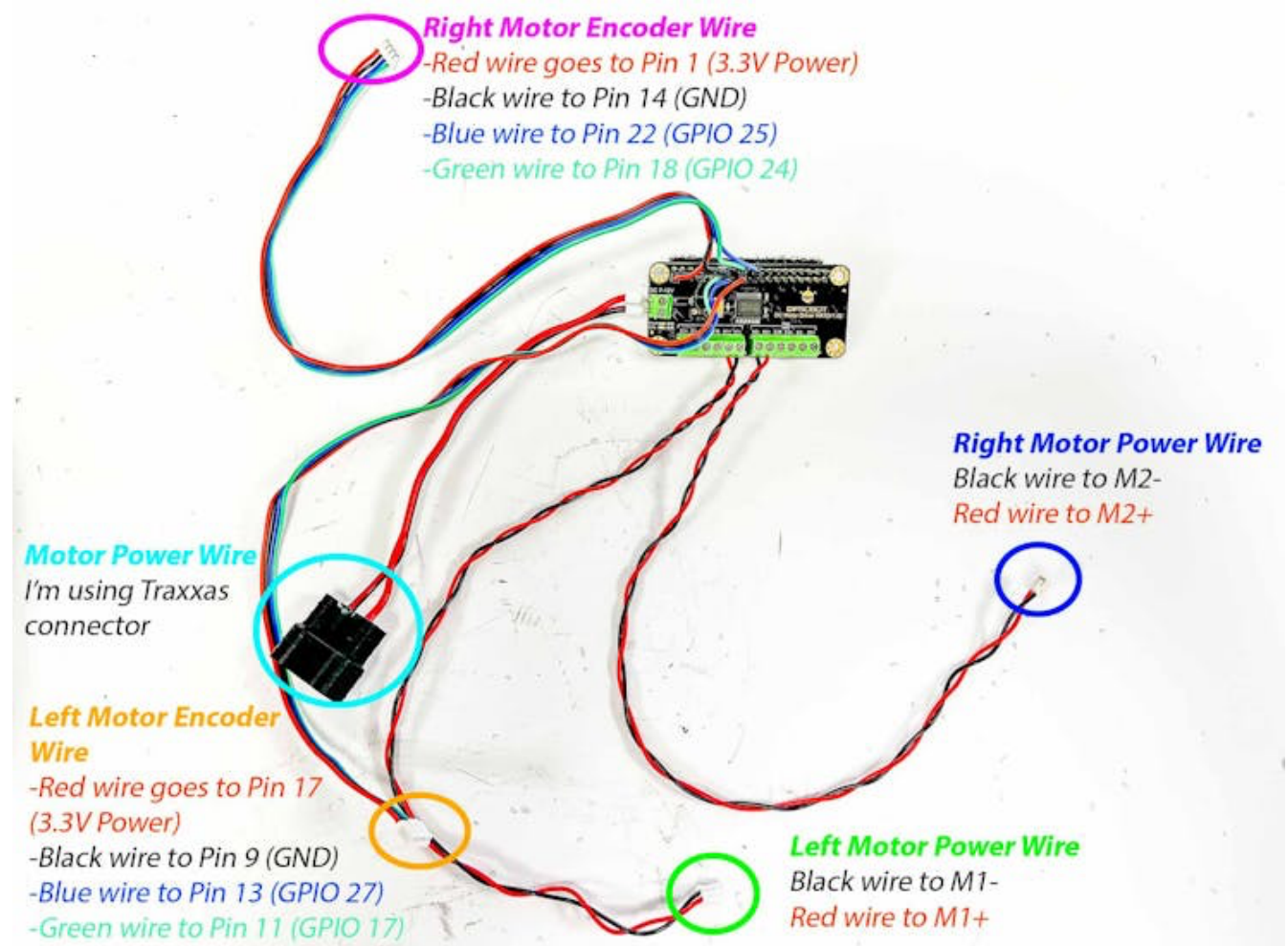


Please take DFRobot HAT Motor driver and wires that you took from motor set.

Follow the Wiring Diagram below to connect all wires on the proper pins. One motor set has two kinds of wires: 2-pin wire to power-up motor, 4-pin wire to power-up encoder and read signal encoder data.



Please follow a Raspberry Pi GPIO diagram to identify the correct pin number.

